

Chapter 5: Energy Storage and Dynamic Circuits

Chapter 5: Outline

Energy Storage and Dynamic Circuits

(Time Varying Characteristics)

Capacitor ↔ Inductor (Dual)

Branch (Device) Equation in Differential Form

Power and Stored Energy

Memory and Continuity

Parallel and Series

Current Divider

Dynamic Circuit (Differential Equation)

Natural Response (No Input, Homogeneous Solution)


Forced Response (Steady State, Particular Solution)

Complete Response = Natural Response + Forced Response

Transient Response, Steady State Response

Capacitor (Brief)

Branch equation

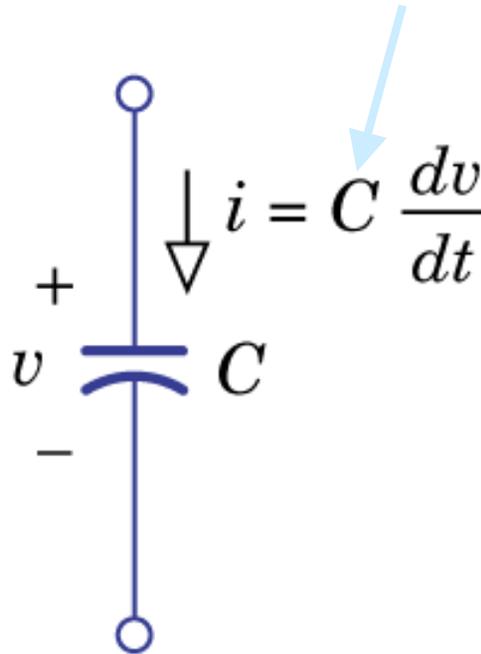

$$\text{instantaneous power : } p = vi = Cv \frac{dv}{dt}$$

$$\text{instantaneous stored energy : } w = \frac{1}{2} Cv^2$$

Electrical memory


$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\mathbf{l}) d\mathbf{l} = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\mathbf{l}) d\mathbf{l}$$

Voltage continuity when the current is finite.

$$v(t_j^+) = v(t_j^-) + \frac{1}{C} \int_{t_j^-}^{t_j^+} i(\mathbf{l}) d\mathbf{l}$$

v_c is the preferred variable.

Inductor (Brief)

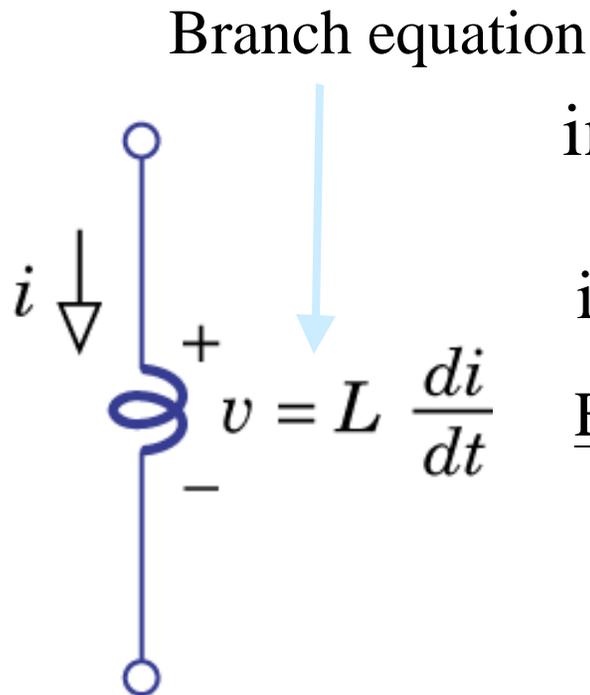

instantaneous power : $p = vi = Li \frac{di}{dt}$

instantaneous stored energy : $w = \frac{1}{2} Li^2$

Electrical memory

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\mathbf{l}) d\mathbf{l} = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\mathbf{l}) d\mathbf{l}$$

Current continuity when the voltage is finite.


i_L is the preferred variable.

Dynamic Circuits


Dynamic Circuits

- A circuit is dynamic when currents or voltages are time-varying.
- Dynamic circuits are described by differential equations.
- Order of the circuit is determined by order of the differential equation.
- The differential equations are derived based on Kirchhoff's laws and device (branch) equations.

First-Order Dynamic Circuits

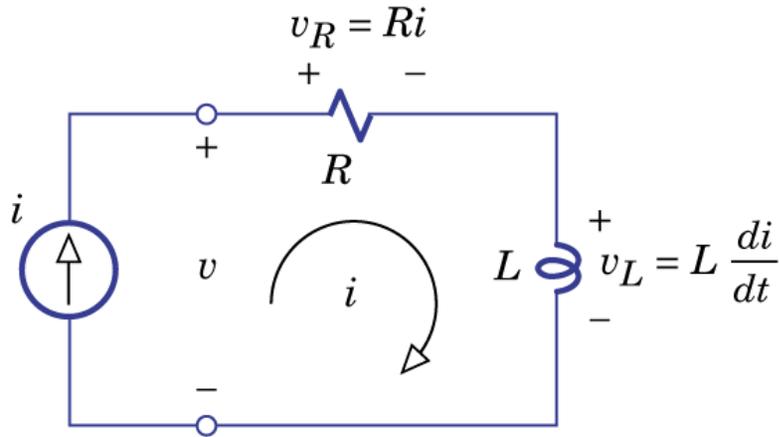

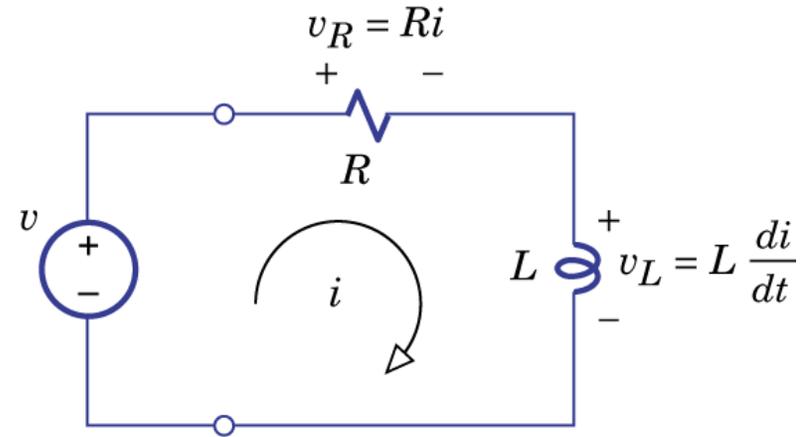(a) Series RL network with a current source



(b) Series RL network with a voltage source


direct form : $v = L \frac{di}{dt} + Ri$

indirect form : $v = L \frac{di}{dt} + Ri$


Generic form (differential): $a_1 \frac{dy}{dt} + a_0 y = f(t)$

← Forcing function

First-Order Circuits

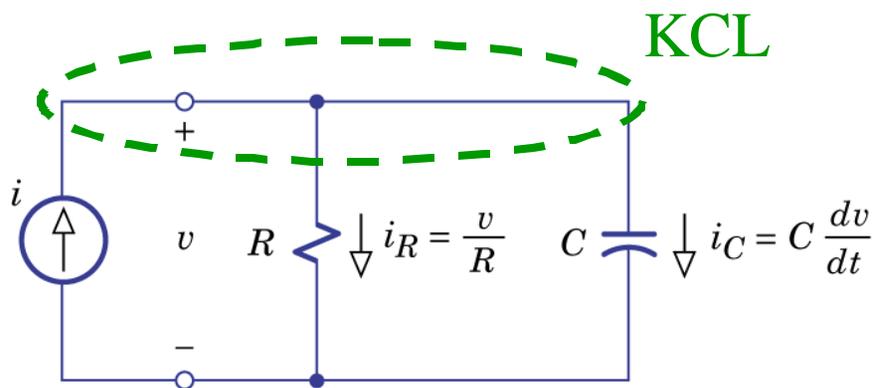

(a) Parallel RC circuit

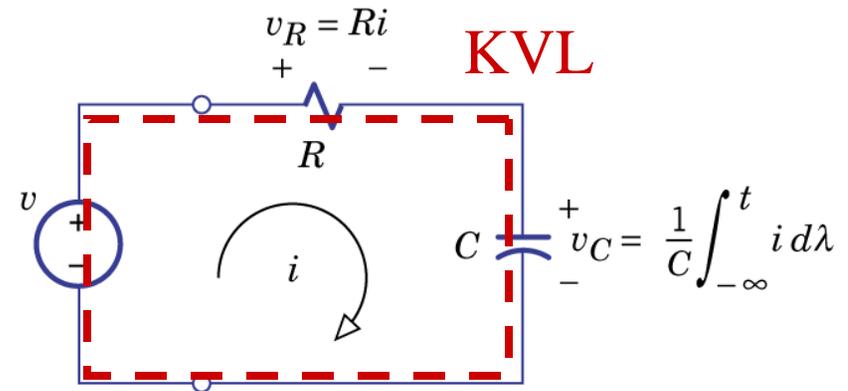

(b) Series RC circuit

$$C \frac{dv}{dt} + \frac{1}{R} v = i$$

$$v = Ri + \frac{1}{C} \int_{-\infty}^t i d\lambda \Rightarrow R \frac{di}{dt} + \frac{1}{C} i = \frac{dv}{dt}$$

$$\text{or } RC \frac{dv_c}{dt} + v_c = v$$


Generally, use v_C or i_L .

Second-Order Circuits

- Second-order circuits: circuits described by a second-order differential equation.

$$\text{Generic form: } a_2 \frac{d^2 y}{dt^2} + a_1 \frac{dy}{dt} + a_0 y = f(t)$$


Second-Order Circuits

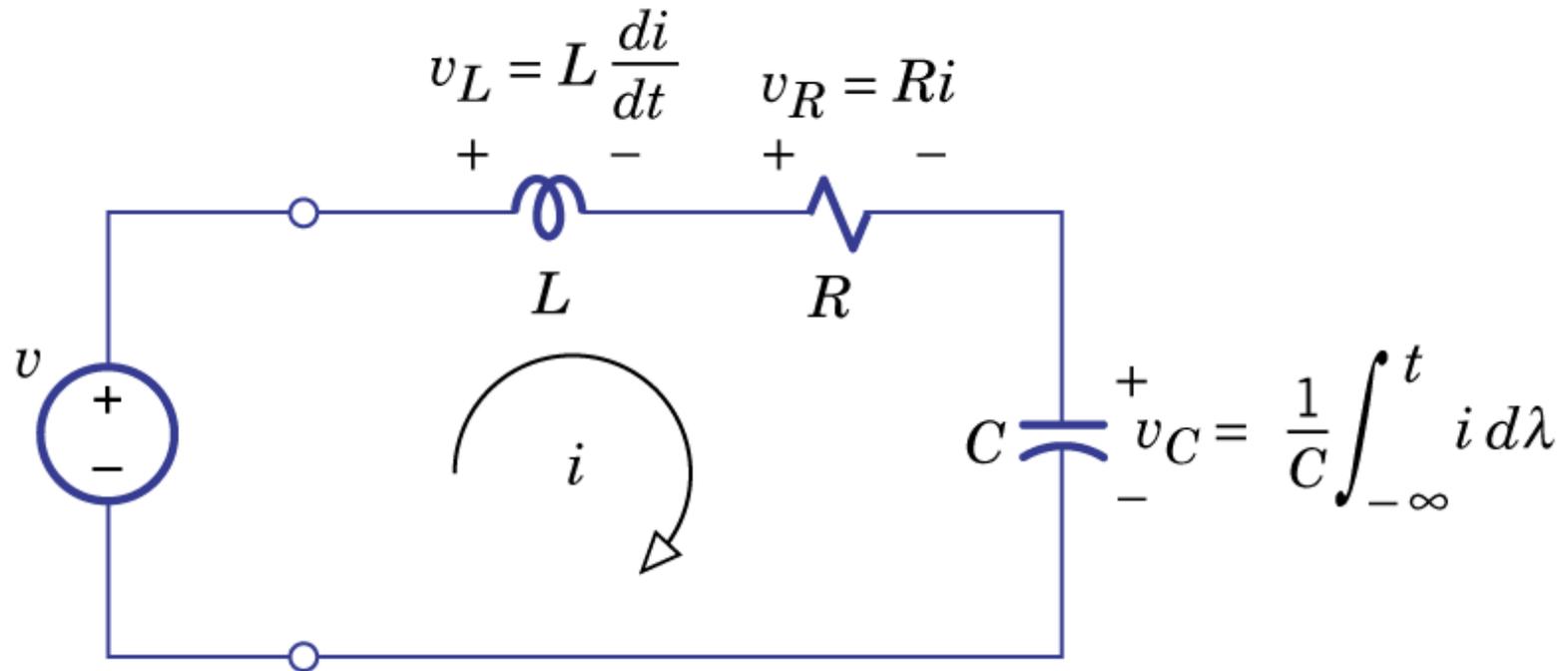

$$\text{KVL : } v = v_L + v_R + v_C$$

$$\text{In differential form : } \frac{dv}{dt} = L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i$$

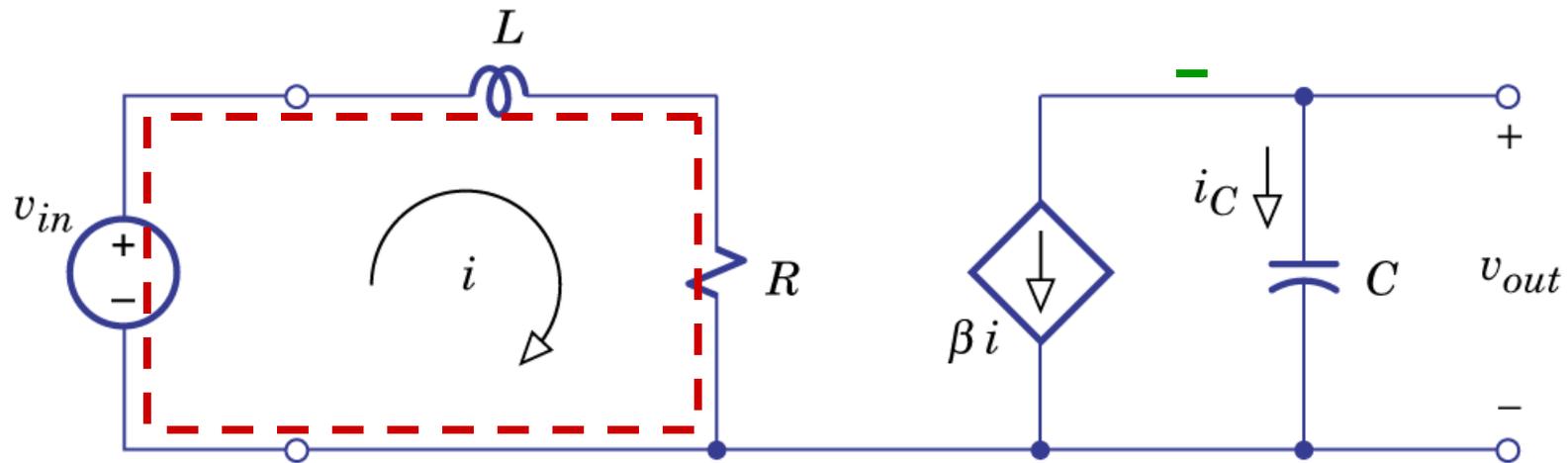Example 5.8: Second-Order Amplifier Circuit



$$v_{in} = L \frac{di}{dt} + Ri$$

$$i = -\frac{C}{b} \frac{dv_{out}}{dt}$$

$$LC \frac{d^2 v_{out}}{dt^2} + RC \frac{dv_{out}}{dt} = -b v_{in}$$

Response:

- Natural, Forced
- Transient, Steady state
- many more,...

Natural Response

- Natural response $y_N(t)$ is the solution of the circuit equation with the forcing function set to zero. It is also known as the complementary solution.
- With the forcing function set to zero, the differential equation becomes homogeneous.
- A homogeneous differential equation can be solved using the characteristic equation along with the initial condition.
- First-order circuits require one initial condition. Second-order circuits require two initial conditions.

First-Order Circuits

$$a_1 \frac{dy_N}{dt} + a_0 y_N = 0$$

Characteristic equation : $a_1 s + a_0 = 0$

$$\Rightarrow s = -\frac{a_0}{a_1}$$

$$y_N(t) = Ae^{st} = Ae^{-\frac{a_0}{a_1}t}$$

A is determined by initial condition $y_N(0^+) = A = Y_0$

Second-Order Circuits

$$a_2 \frac{d^2 y_N}{dt^2} + a_1 \frac{dy_N}{dt} + a_0 y_N = 0$$

Characteristic equation : $a_2 s^2 + a_1 s + a_0 = 0$

$$\Rightarrow s = \mathbf{a}_1, \mathbf{a}_2 \left(\frac{-a_1 \pm \sqrt{a_1^2 - 4a_2 a_0}}{2a_2} \right)$$


$$y_N(t) = A_1 e^{a_1 t} + A_2 e^{a_2 t}$$

A_1, A_2 are determined by two initial conditions $y_N(0^+)$ and $\frac{dy_N(0^+)}{dt}$

Stable Circuit

- A circuit is stable if the circuit variable $y_N(t) \rightarrow 0$, as $t \rightarrow \infty$.
- A circuit is exponentially stable if the circuit variable $y_N(t) \rightarrow 0$, as $t \rightarrow \infty$ in an exponential form.

Example 5.9: Capacitor Discharge

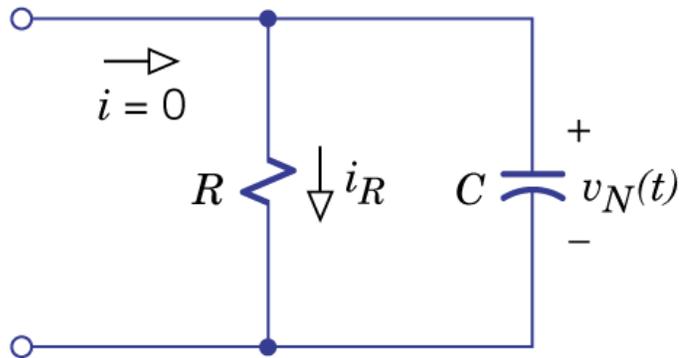

$$C = 300 \text{ mF}$$

$$R = 2 \text{ MW}$$

$$v(0^-) = 1000 \text{ V}$$


$$RC \frac{dv_N}{dt} + v_N = 0$$

$$RCs + 1 = 0 \Rightarrow s = -\frac{1}{RC} = -\frac{1}{600}$$

$$v_N(t) = Ae^{-t/600}$$

$$A = v_N(0^+) = v_N(0^-) = 1000 \text{ (continuity)}$$
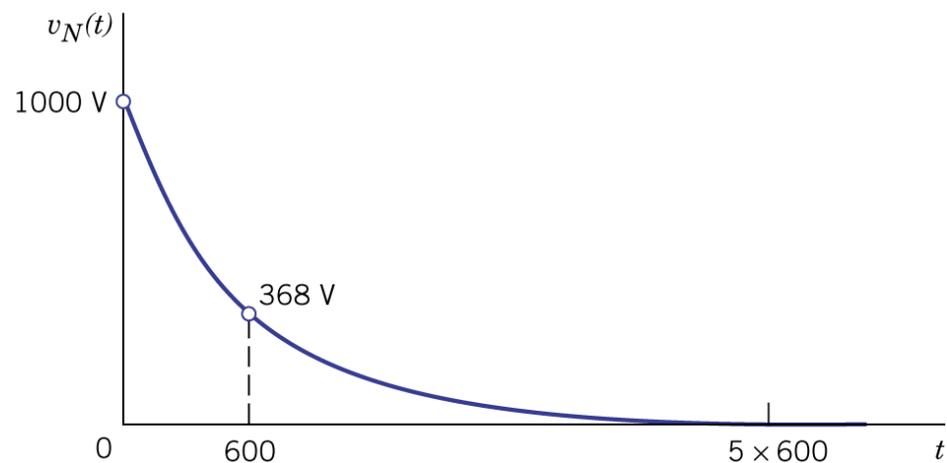
$$v_N(t) = 1000e^{-\frac{t}{600}} \text{ V}, t > 0$$



Forced Response


- Forced response $y_F(t)$ is the solution of the inhomogeneous differential equation (i.e., the forcing function is not zero), independent of any initial conditions. The solution is also known as the particular solution.
- Please refer to Table 5.3 for method of undetermined coefficients.

Table 5.3

TABLE 5.3 Selected Trial Solutions for Forced Response

$f(t)$	$y_F(t)$
k_0 (a constant)	K_0 (a constant)
$k_1 t$	$K_1 t + K_0$
$k_2 e^{at}$	$K_2 e^{at}$
$k_3 \cos \omega t + k_4 \sin \omega t$	$K_3 \cos \omega t + K_4 \sin \omega t$

Example 5.10 Sinusoidal Forced Response

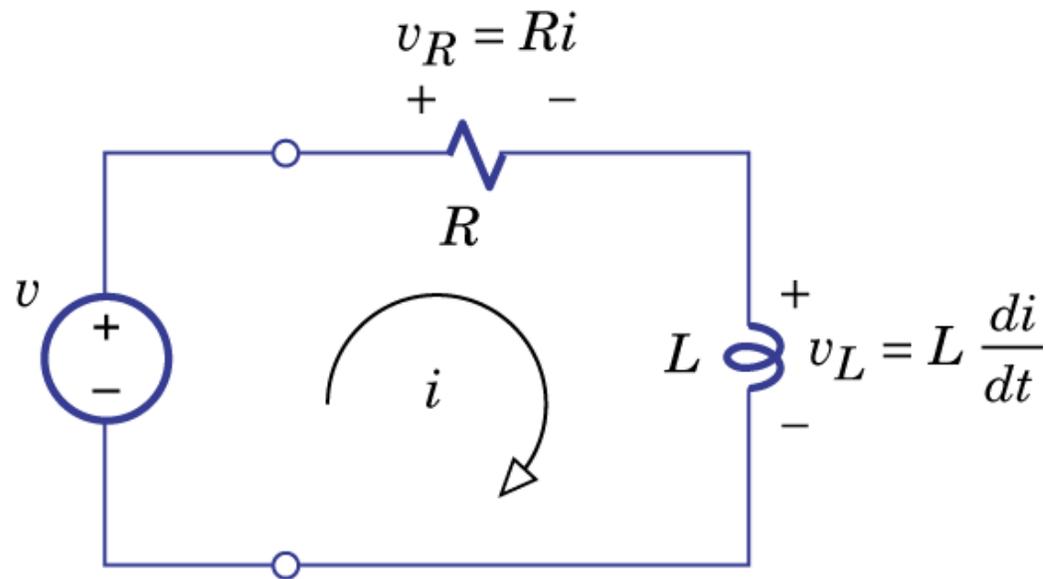

(b) Series RL network with a voltage source

$$R=4\Omega$$

$$L=0.1H$$

$$V(t)=25\sin 30t$$


Example 5.10 Sinusoidal Forced Response

$$0.1 \frac{di_F}{dt} + 4i_F = 25 \sin 30t$$

$$i_F(t) = k_3 \cos 30t + k_4 \sin 30t$$

after substitution, we have $k_3 = -3, k_4 = 4$
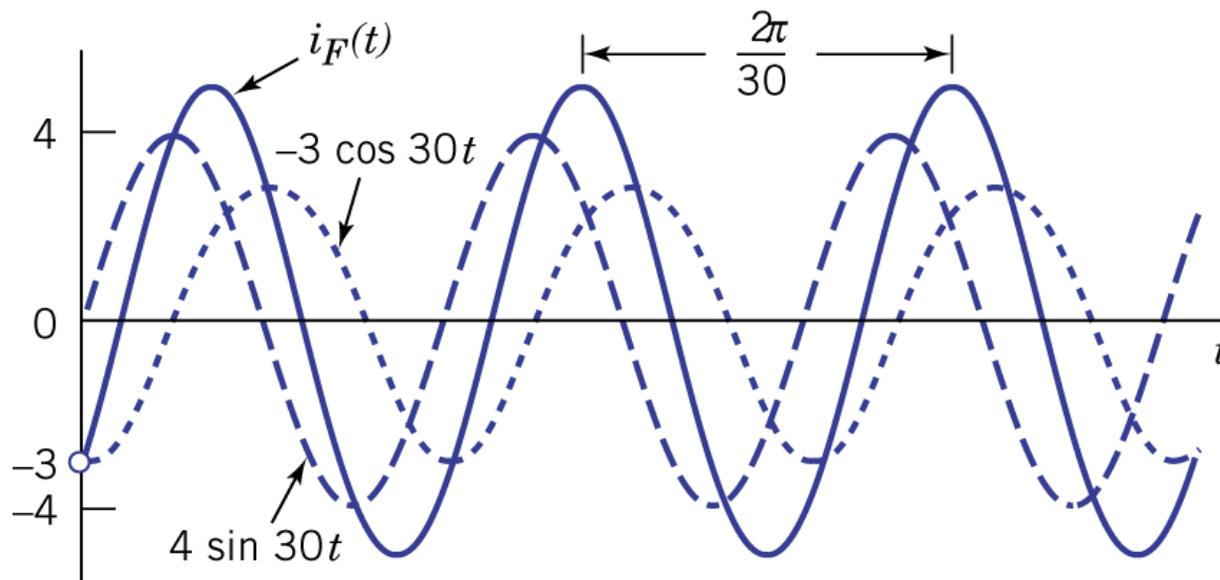
$$i_F(t) = -3 \cos 30t + 4 \sin 30t \quad (\text{or } i_F(t) = A \cos(30t + \mathbf{q}))$$



If the forcing function contains any term proportional to a component of the natural response (i.e., excitation of a natural frequency), then the term must be multiplied t .

Example 5.11: Exponential Forced Response

$$0.1 \frac{di}{dt} + 4i = v$$

homogeneous solution : $0.1s + 4 = 0 \Rightarrow s = -40$

$$v = 10e^{-bt}$$

if $b = 20$

$$i_F(t) = k_2 e^{-20t}$$

$$k_2 = 5$$

$$i_F(t) = 5e^{-20t} \text{ A}$$

if $b = 40$

$$i_F(t) = k_2 t e^{-40t}$$

$$k_2 = 100$$

$$i_F(t) = 100t e^{-40t} \text{ A}$$

Complete Response

- Complete response is the sum of the natural response and the forced response, i.e., $y(t) = y_F(t) + y_N(t)$.
- The constants in $y_N(t)$ are evaluated from the initial conditions on with the complete response.
- For a stable circuit, $y(t) = y_F(t)$, as $t \rightarrow \infty$, since $y_N(t) \rightarrow 0$, as $t \rightarrow \infty$.
- The circuit is in the steady state if $y_N(t)$ is negligible compared to $y_F(t)$.
- Before arriving the steady state, the circuit is in the transient state.

Example 5.12: Complete Response Calculation (RL)

$$0.1 \frac{di}{dt} + 4i = v, \quad i(t) = 0 \text{ for } t < 0$$

$$v(t) = 400 \sin 280t, \text{ for } t > 0$$

$$\text{homogeneous solution : } i_N(t) = Ae^{-40t}$$


$$\text{particular solution : } i_F(t) = -14 \cos 280t + 2 \sin 280t$$

$$\text{complete response : } i(t) = i_N(t) + i_F(t) = Ae^{-40t} - 14 \cos 280t + 2 \sin 280t$$

$$i(0^+) = 0 = -14 + A$$

$$A = 14$$

Example 5.12: Complete Response Calculation (RL)

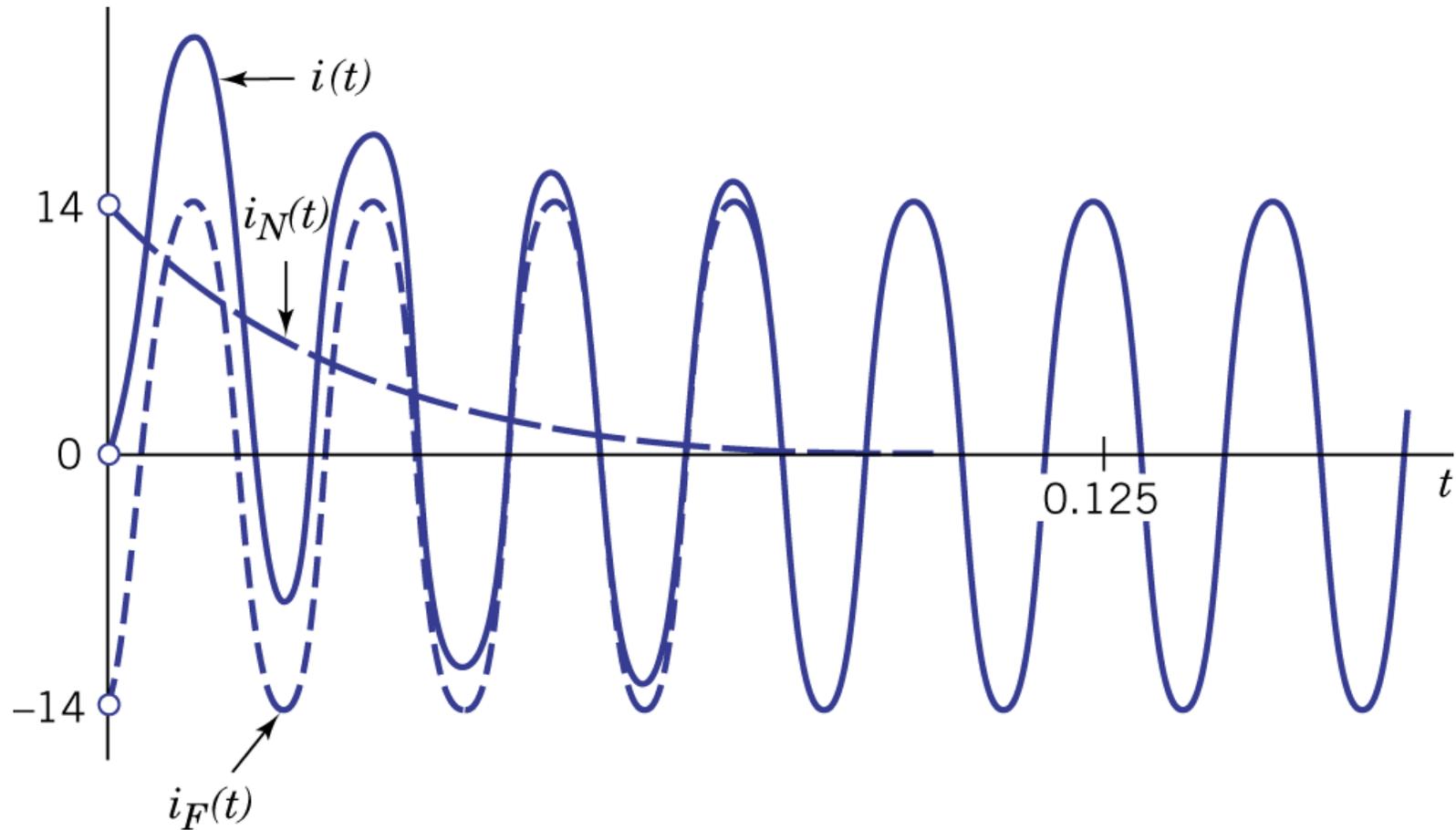

Chapter 5: Problem Set

- 42, 44, 45, 48, 54, 61, 64